 


Делитель сигнала / частоты на 8



```

module freg_div8
(
    output led0,
    input clk,
    output reg counter = 1'b0
);

assign led0 = counter;
reg[2:0] count8;

always @(posedge clk)
begin
    count8=count8+1;
    if (count8==0) counter = !counter;
end
endmodule

```

